

1. For the circuit in Figure 1, use mesh analysis to find the power absorbed by the  $2\ \Omega$  resistor.

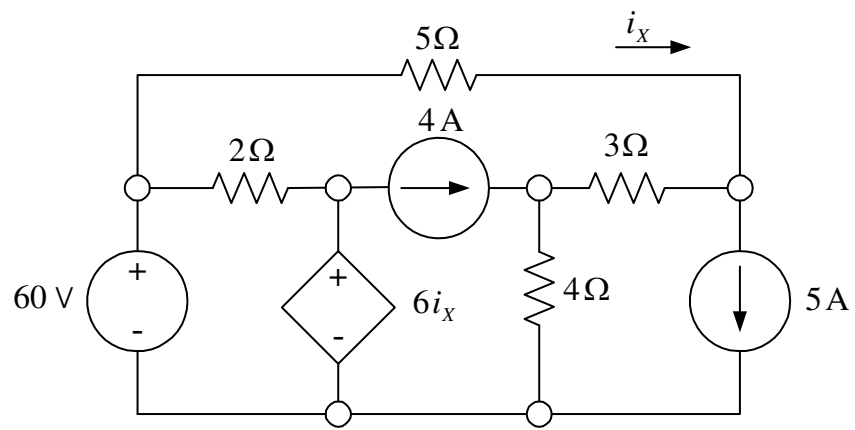


Figure 1