

Test I

(1) For the circuit in Figure 1 use node analysis to find the voltage v_x and the power supplied by the dependent current source. (10)

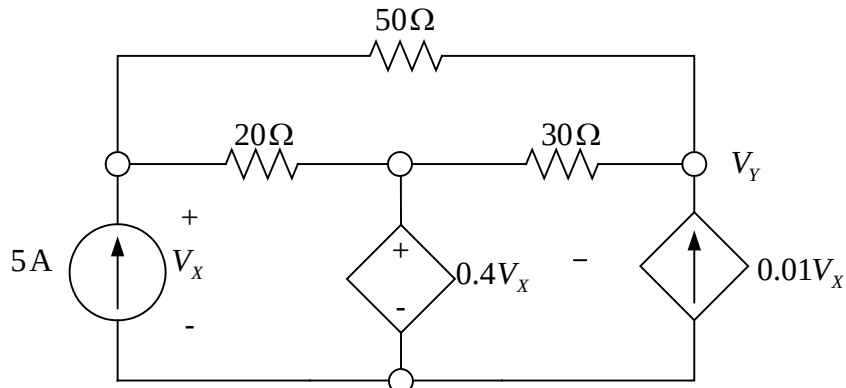


Figure 1

Sol.

KCL left node

$$\frac{V_x - V_y}{50} + \frac{0.6V_x}{20} = 5$$

or

$$2V_x - 2V_y + 3V_x = 500 \rightarrow 5V_x - 2V_y = 500 \quad (1)$$

KCL right node

$$\frac{V_x - V_y}{50} + \frac{V_y - 0.4V_x}{30} - 0.01V_x = 0$$

or

$$3V_y - 3V_x + 5V_y - 2V_x - 1.5V_x = 0 \rightarrow -6.5V_x + 8V_y = 0 \quad (2)$$

Solve

$$V_x = \frac{\begin{vmatrix} 500 & -2 \\ 0 & 8 \end{vmatrix}}{\begin{vmatrix} 5 & -2 \\ -6.5 & 8 \end{vmatrix}} = \frac{4000}{27} = 148.15 \text{ V}$$

From (1) or (2),

$$V_y = \frac{5V_x - 500}{2} = 120.37 \text{ V} \text{ or } V_y = \frac{6.5}{8}V_x = 120.37 \text{ V}$$

(2) For the circuit in Figure 2 find values for i_L and v_X at :

(10)

- $t = 0^-$
- $t = 0^+$
- $t = \text{infinity } (\infty)$
- $t = 0.2 \text{ ms}$

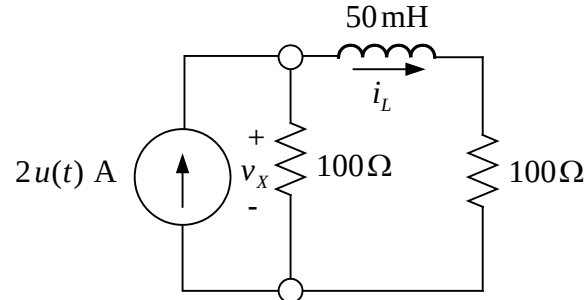


Figure 2

Sol.

- $t = 0^-, i_L = 0 \text{ A}, v_X = 0 \text{ V}$
- $t = 0^+, i_L = 0 \text{ A}, v_X = 200 \text{ V}$
- $t = \text{infinity } (\infty), i_L = 1 \text{ A}, v_X = 100 \text{ V}$

$$\tau = \frac{50 \times 10^{-3}}{200} = \frac{1}{4} \text{ ms}$$

$$\therefore i_L = 1(1 - e^{-4000t})u(t) \text{ A}$$

$$i_L(0.2\text{ms}) = 1(1 - e^{-4000(0.2 \times 10^{-3})})(1) = 0.5507 \text{ A}$$

$$v_X(0.2\text{ms}) = 100(100 - e^{-4000(0.2 \times 10^{-3})})(1) = 144.93 \text{ V}$$

(1) For the circuit in Figure 1 use superposition to find the voltage V . (10)

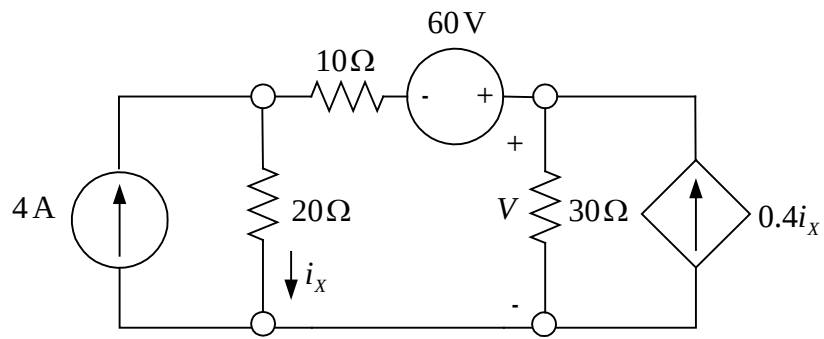


Figure 1