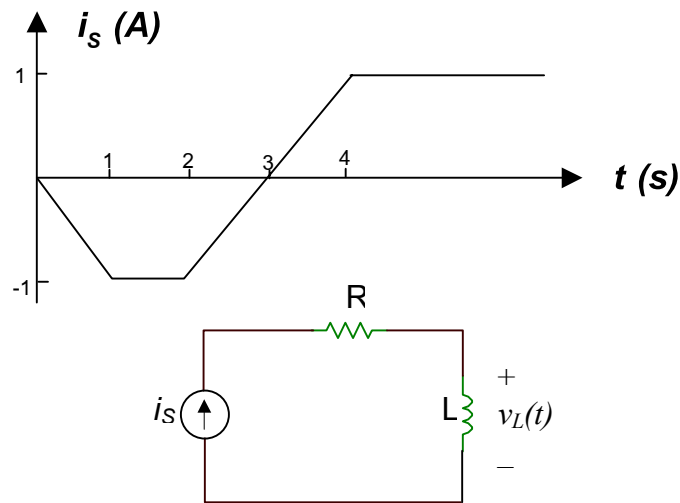


1. For the circuit and independent current as shown below.



- If  $R = 2 \, \Omega$  and  $L = 4 \, \text{H}$  determine and sketch the voltage  $v_L(t)$  for  $t > 0$ , assume that the inductor current  $i_L(0) = 0$ .
- Determine and sketch the power absorbed by the inductor  $p_L(t)$  for  $t > 0$ .
- Determine the energy stored in the inductor at  $t = 1.5 \, \text{s}$  and at steady state.
- If the inductor in the above circuit is replaced by a capacitor  $C = 1 \, \text{F}$  determine the voltage across the capacitor  $v_C$  at  $t = 3 \, \text{s}$ , assume that the capacitor voltage  $v_C(0) = 2 \, \text{V}$ .